

EXPERIMENT NO: 9

Title: To implement :i) Serial In Parallel Out (SIPO) register and ii) Johnson counter using simulator

EXPERIMENT NO: 9

Simulate a Serial In Parallel Out (SIPO) register and Johnson counter

Name: Hayden Cordeiro

SECOMPS

RollNo: 05

AIM	To implement a Serial In Parallel Out (SIPO) register and Johnson counter using simulator
LEARNING OBJECTIVE	To explore a simulation tool for computer organization components.
LEARNING OUTCOME	Students can simulate the operation of multiplier unit .
LAB OUTCOME	CSL403.2: Ability to estimate the output of computer hardware operations using simulator.
PROGRAM OUTCOME	PO11, PO32, PO41, PO52, PO83, PO9-3, PO12-2, PS011
BLOOM'S TAXONOMY LEVEL	Evaluate
THEORY	<p>Note for students: Students are supposed to write the theory related to Serial In Parallel Out (SIPO) register and Johnson counter and explain its working.</p> <p>SIPO: A serial-in, parallel-out shift register is similar to the serial-in, serial-out shift register in that it shifts data into internal storage elements and shifts data out at the serial-out, data-out, pin. It is different in that it makes all the internal stages available as outputs. Therefore, a serial-in, parallel-out shift register converts data from serial format to parallel format.</p> <p>Working: In Serial In Parallel Out (SIPO) shift registers, the data is stored into the register serially while it is retrieved from it in parallel-fashion. The data word which is to be stored (Data in) is fed serially at the input of the first flip-flop (D1 of FF1). It is also seen that the inputs of all other flip-</p>

flops (except the first flip-flop FF1) are driven by the outputs of the preceding ones say for example, the input of FF2 is driven by the output of FF1. In this kind of shift register, the data stored within the register is obtained as a parallel-output data word (Data out) at the individual output pins of the flip-flops (Q1 to Qn). In general, the register contents are cleared by applying high on the clear pins of all the flip-flops at the initial stage. After this, the first bit, B1 of the input data word is fed at the D1 pin of FF1. This bit (B1) will enter into FF1, get stored and thereby appears at its output Q1 on the appearance of first leading edge of the clock. Further at the second clock tick, the bit B1 right-shifts and gets stored into FF2 while appearing at its output pin Q2 while a new bit, B2 enters into FF1. Similarly at each clock tick the data within the register moves towards right by a single bit while a new bit of the input word enters into the register. Meanwhile one can extract the bits stored within the register in parallel-fashion at the individual flip-flop outputs.

JOHNSON COUNTER:

Johnson Counter. A Johnson counter is a modified ring counter in which the output from the last flip flop is inverted and fed back as an input to the first. It is also called as Inverse Feedback Counter or Twisted Ring Counter.

A Johnson counter is a modified ring counter, where the inverted output from the last flip flop is connected to the input to the first. The register cycles through a sequence of bit-patterns. The MOD of the Johnson counter is $2n$ if n flip-flops are used. The main advantage of the Johnson counter counter is that it only needs half the number of flip-flops compared to the standard ring counter for the same MOD.

It can be implemented using D-type flip-flops (or JK-type flip-flops).

Working:

The default state of Johnson counter is 0000 thus before starting the clock input we need to clear the counter using clear input.

Whenever a clock edge hits the counter the output of each flip-flop will transfer to the next stage (flip-flop) but the inverted output of the last flip-flop will shift to the first stage making the state 1000.

Upon next clock cycle, another '1' will stack in from the left side as the inverted output of the last stage will be shifted to the first stage.


On next clock cycle, another '1' will add in from left until the state becomes 1111.

Now that the last flip-flop's output is '1', the next clock cycle will shift the invert of the last flip-flop which is '0' into the first flip-


flop. It will result in stacking '0' from the left side. This stacking of the first 0 will make the state 1111 into 0111. The next coming clock cycles will stack in 0's from the left making the states 0011, 0001 & 0000 with each clock cycle. Eventually, it reaches its default state and it starts from the beginning again.

CIRCUIT DIAGRAM

SIPO register:

 

Johnson Counter:

 

COMPONENTS USED


- To build any register or counters, we need :
- 1. FlipFlops.
 - 2. LogicGates.
 - 3. Wires toconnect.

STEPS TO DESIGN THE CIRCUIT	<p>Start the simulator as directed. This simulator supports 5 valued logic.</p> <ol style="list-style-type: none"> 1. To design a 4 bit shift register (right shift), we need 4 MSD flip flop, 1 free running clock, 1 Bit switch (which will act as input to the left most flip flop), 4 Bit display (to see the output of individual flip flops so that the shifting can be seen with the clock input), wires. 2. The MSD flip flop component is in the sequential circuit drawer in the pallet. The pin configuration is shown whenever the mouse is hovered on any canned component of the palette or press the 'show pin config' button. Pin numbering starts from 1 and from the bottom left corner (indicating with the circle) and increases anticlockwise. 3. For MSD flip flop input is in pin 5, output (Q) is in pin 4, clock is in pin 8 4. click on the MSD flip flop component in the pallet and then click on the position of the editor window where you want to add the component (no drag and drop, simple click will serve the purpose), likewise add 4 MSD flip flops, 1 free running clock, 1 Bit switch and 4 bit Displays (from Display and Input drawer of the pallet, if it is not seen scroll down in the drawer) 5. To connect any two components select the Connection menu of Palette, and then click on the Source terminal and click on the target terminal. connect all the components, connect the clock to the pin-8 of all the MSD flip flops, connect a bit switch to the pin-5 (Q) of the left most MSD flip flop, connect 4 bit display to the pin-4 of 4 MSD flip flops, connect the Q output of the previous flip flop to the D (pin 5) input of the next flip flop.
--	--


6. To see the circuit working, click on the Selection tool in the pallet then give input by double clicking on the bit switch, to the left most D flip flop at pi-5 (let it be 1), start the clock now check the output and see how the 1 is shifting from left to right.
7. Similar way counter can be implemented.

SIMULATED RESULTS

Johnsons counter:

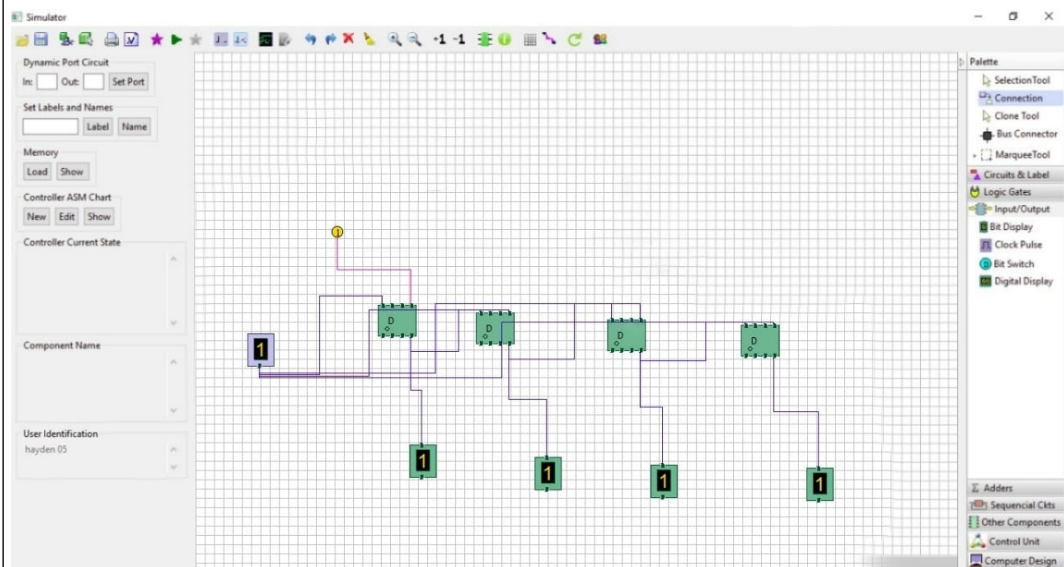

SERIAL IN PARALLEL OUT :

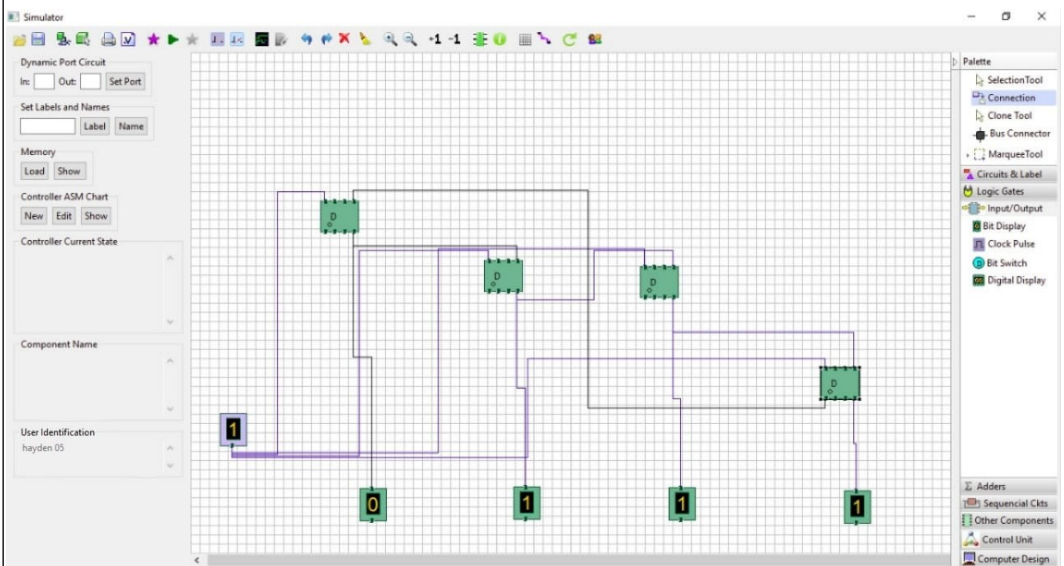

CONCLUSION	We have successfully implemented and simulated serial in parallel out register and johnsons counter
REFERENCES	https://cse.iitkgp.ac.in/~chitta/coldvl/rca_design.html